

[8] Seat No.: _____

No. of printed pages: 02

SARDAR PATEL UNIVERSITY
BCA SEM-I EXAMINATION 2017 (NC)
Digital Computer Electronics (US01EBCA01)

Time: 2:00 p.m. to 4:00 p.m.

Date: 17/02/2017, Friday

Total Marks: 70

Q.1 Multiple Choice Questions

[10]

- 1 The _____ gate has two or more input signals. All inputs must be high to get a high output.
[A. AND B. OR C. NAND D. NOR]
- 2 De Morgan's first theorem says that a NOR gate is equivalent to a _____.
[A. bubbled OR B. bubbled NOR C. bubbled AND D. AND bubbled]
- 3 A _____ is a combinational circuit that converts binary information from the $2n$ coded inputs to an n outputs.
[A. Half Adder B. Decoder C. Encoder D. Comparator]
- 4 In k-map, pair eliminates _____ variable.
[A. one B. two C. three D. four]
- 5 In Comparator, _____ gate is use for comparing bits in word.
[A. AND B. XOR C. NOR D. XNOR]
- 6 A combinational circuit that performs the arithmetic addition of two bits is called _____.
[A. Full Adder B. Binary Adder C. Half Adder D. Decoder]
- 7 Half adder consist of _____ & _____ Gates.
[A. XOR, AND B. XOR, OR C. XNOR, AND D. XNOR, OR]
- 8 In D flip-flop, when CLK is low then input is _____.
[A. high B. Don't care C. low D. Not change]
- 9 A register is a group of _____ that work together as a unit.
[A. multiplexer B. decoder C. flip-flop D. gates]
- 10 A multiplexer is also called a _____.
[A. data multiplier B. data selector C. data inverter D. data remover]

Q.2 Write Short Questions. [Any 10] [20]

- 1 Prepare truth table for: $\overline{AB} + \overline{BC}$
- 2 Write **Distributive Law** for addition and multiplication.
- 3 Prove that **NAND Gate** is equivalent to **Bubbled OR Gate** using Truth table.
- 4 Draw **K-Map** for 3 variables and randomly show **pair and quade** in same.
- 5 Draw circuit of **Comparator**.
- 6 Explain **Sum of Product**.
- 7 Draw circuit of **Half Adder**.
- 8 Draw Truth table for 3 input **Full Adder** showing carry and sum.
- 9 Write a note on **Multiplexer** without circuit.
- 10 Draw circuit and truth table for **unlocked D Flip-Flop**.
- 11 Differentiate between **Shift Left** and **Shift Right Register** with proper example.
- 12 Write a note on **Controlled Buffer Register**.

Q.3(A) Write a detail note on following gates: AND, NAND, Bubbled AND [06]
(B) Prove that $ABC + \overline{A}BC = AB$ using truth table. [04]

OR

Q.3(A) Write a detail note **De'Morgans Theorem**. [06]
(B) Simplify Boolean expression and draw circuit. $A.B + C.D + A.B + C.D$ [04]

Q.4(A) Explain **8X3 Encoder**. [06]
(B) Define **K-Map**. Explain with proper example how it is used to reduced equation. [04]

OR

Q.4(A) Explain **3X8 Decoder**. [06]
(B) Define **K-Map**. Also explain **PAIR** in context of same. [04]

Q.5(A) Write a detail note on **4-bit Binary Adder** with Circuit Diagram. [06]
(B) Explain working of **Half Adder**. [04]

OR

Q.5(A) Write a detail note on **4-bit Binary Subtractor** with Circuit Diagram. [06]
(B) Explain working of **Full Adder**. [04]

Q.6 Write a detail note on **Shift Registers**. Also discuss **Counters**. [10]

OR

Q.6 Define **FlipFlop**. Also discuss **D Latches (clocked and unclocked)**. [10]

— X —
(2)