

[33]

SARDAR PATEL UNIVERSITY**BCA Semester-3 On-Demand Examination [NC], February- 2024.
US03BCA51 || DIGITAL COMPUTER ELECTRONICS**

Date: 20/02/2024

Time : 02.00 p.m. – 04.00 p.m.

Marks: 50

Q-1 Select the appropriate option for the following questions:**10**

- 1) The OR gate has two or more input signals. If any input is _____, the output is high.
A. High C. Both A and B
B. Low D. None
- 2) De Morgan's second theorem says that a NAND gate is equivalent to a _____.
A. bubbled AND C. OR bubbled
B. bubbled NAND D. bubbled OR
- 3) In k-map, quad eliminates _____ variable.
A. One C. Two
B. Three D. Four
- 4) A _____ is a combinational circuit that converts binary information from the 2^n coded inputs to n outputs.
A. Half Adder C. Encoder
B. Decoder D. Comparator
- 5) A combinational circuit that performs the arithmetic addition of two bits is called _____.
A. full adder C. binary adder
B. half adder D. decoder
- 6) A multiplexer also called a _____.
A. data multiplier C. data inverter
B. data selector D. data remover
- 7) In shift right register, the arrival of the first rising clock edge sets the _____ flip-flop.
A. Left C. Up
B. Right D. Down
- 8) A _____ register is the simplest kind of register; all it does store a digital word.
A. Shift left C. Buffer
B. Shift Right D. Simple
- 9) In D flip-flop, when CLK is low then input is _____.
A. High C. Don't care
B. Low D. No change
- 10) The relationship between a function and its binary variables can be represented in _____.
A. Truth table C. Encoder
B. Decoder D. Multiplexer

Q-2 Give short answers of the following questions: (ANY Eight)**16**

- 1) Explain NOT, XOR gate.
- 2) Write truth table for : $A'B+B'C$
- 3) Define comparator in short.
- 4) Define Flip flop. What is Race condition?

(1)

(P.T.O.)

- 5) What is De-Multiplexer?
- 6) Define parity bit. What is odd and even parity?
- 7) Give example of 4 bit binary subtraction.
- 8) What is register? Draw circuit diagram of shift right register.
- 9) Simplify using k-map $F(A,B,C)=\Sigma(1,2,5)$.
- 10) Simplify Boolean expression and draw circuit. $AB+CD+AB+CD$.

Q3 Explain Basic gates. 06

OR

Q3 Explain de morgan's first and second theorem. 06

Q4 What is k-map? Explain pair and quad with example. 06

OR

Q4 Explain 8x3 line encoder in detail. 06

Q5 Explain 4*1 Multiplexer. 06

OR

Q5 Explain Half adder and Full adder in detail. 06

Q6 Explain controlled buffer register. 06

OR

Q6 Explain Ring Counter. 06

—X—

(2)